

Prelab #2

```
In [37]: import jlab as jl
         from importlib import reload
         reload(jl)
```

```
Out[37]: <module 'jlab' from '/Users/n1le/Documents/Classes/PHYS 3330/jlab.py'>
```

Section 2.2, Voltage Dividers

2.2.1 What is the current I through each resistor in a voltage divider?

$$I = V/R = V_{in}/(R_1 + R_2)$$

2.2.2 What is the voltage across R_2 ? Express WRT current.

The current is constant in a voltage divider, so $I = V_{in}/(R_1 + R_2)$ and we can then calculate the voltage from Ohm's Law: $V_{out} = IR = V_{in}R_2/(R_1 + R_2)$. This is V_{out} since it's the voltage coming out of the top resistor with respect to ground (0V).

2.2.3 As above, $V_{out} = V_{in}R_2/(R_1 + R_2)$. The following code calculates the output voltages at each node of a voltage divider. Parameters:

- v_{in} (float): The input voltage in volts.
- resistors (list): A list of resistance values in ohms.


Returns:

- list: A list of output voltages at each node in volts.


```
def voltage_divider(v_in: float, resistors: list) -> list:
    total_resistance = sum(resistors)
    voltages = []
    v_out = v_in
    for r in resistors:
        v_drop = v_out * (r / total_resistance)
        voltages.append(v_drop)
        v_out -= v_drop
        total_resistance -= r
    return voltages
```

2.2.4 Build the circuit


(a)

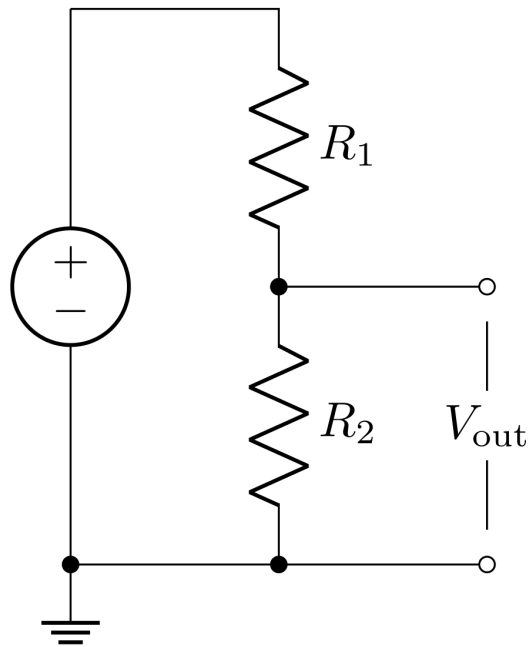

(b)

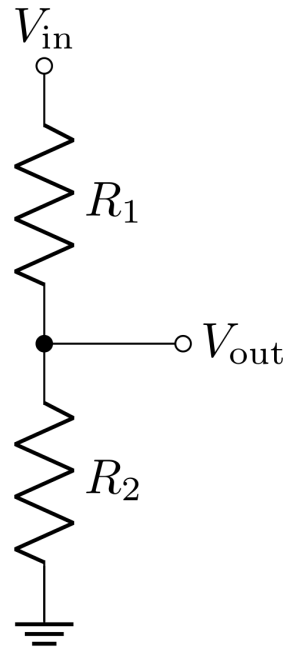

(c)

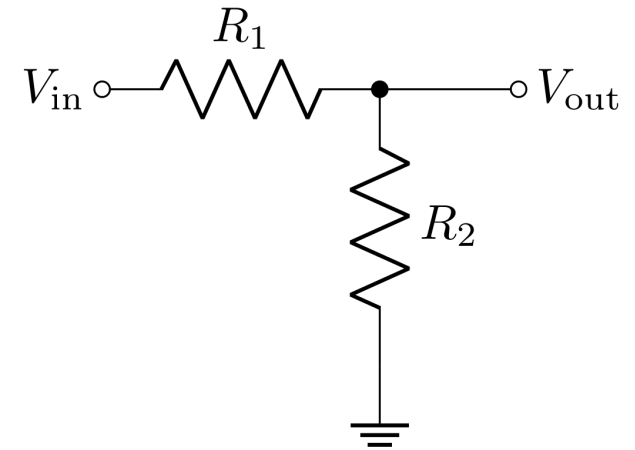

in LTSpice with

- $V_{in} = 10V$
- $R_1 = 1k\Omega$
- $R_2 = 3k\Omega$. Calculate I and V_{out} using results from the previous questions, then run a simulation to measure the two.

Numerically: $V_{out} = V_{in}R_2/(R_1 + R_2) = 7.5V$, $I = V_{in}/(R_1 + R_2) = 10/4 \cdot 10^3 = 2.5 \cdot 10^{-2}A = 2.5mA$


```
In [38]: vin = 10.0
r1 = 1 * 10**3 # 1 kOhm
r2 = 3 * 10**3 # 3 kOhm
jl.voltage_divider(vin, [r1, r2])
```

```
Out[38]: [7.5]
```

Code, numerical solutions, and simulation all agree!



.op

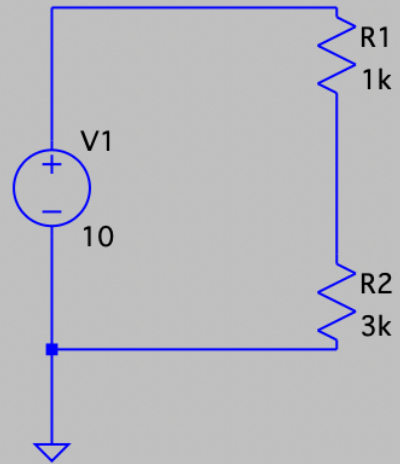



Section 2.3, Transfer Function

2.3.1 Write down the equation for the transfer function of the ideal voltage divider.

$$T = \frac{V_{out}}{V_{in}} = \frac{V_{in}R_2/(R_1+R_2)}{V_{in}} = \frac{R_2}{(R_1+R_2)}$$

2.3.2 For $R_1 = 2k\Omega$ and $R_2 = 1k\Omega$, what is the value of the transfer function?

Simply plugging in values: $T = \frac{1k\Omega}{3k\Omega} = \frac{1}{3}$


```
In [39]: r1 = 2 * 10**3 # 2 kOhm
r2 = 1 * 10**3 # 1 kOhm
jl.transfer_function_voltage_divider([r1, r2])
```


```
Out[39]: [0.3333333333333333]
```

Calculated and code match!

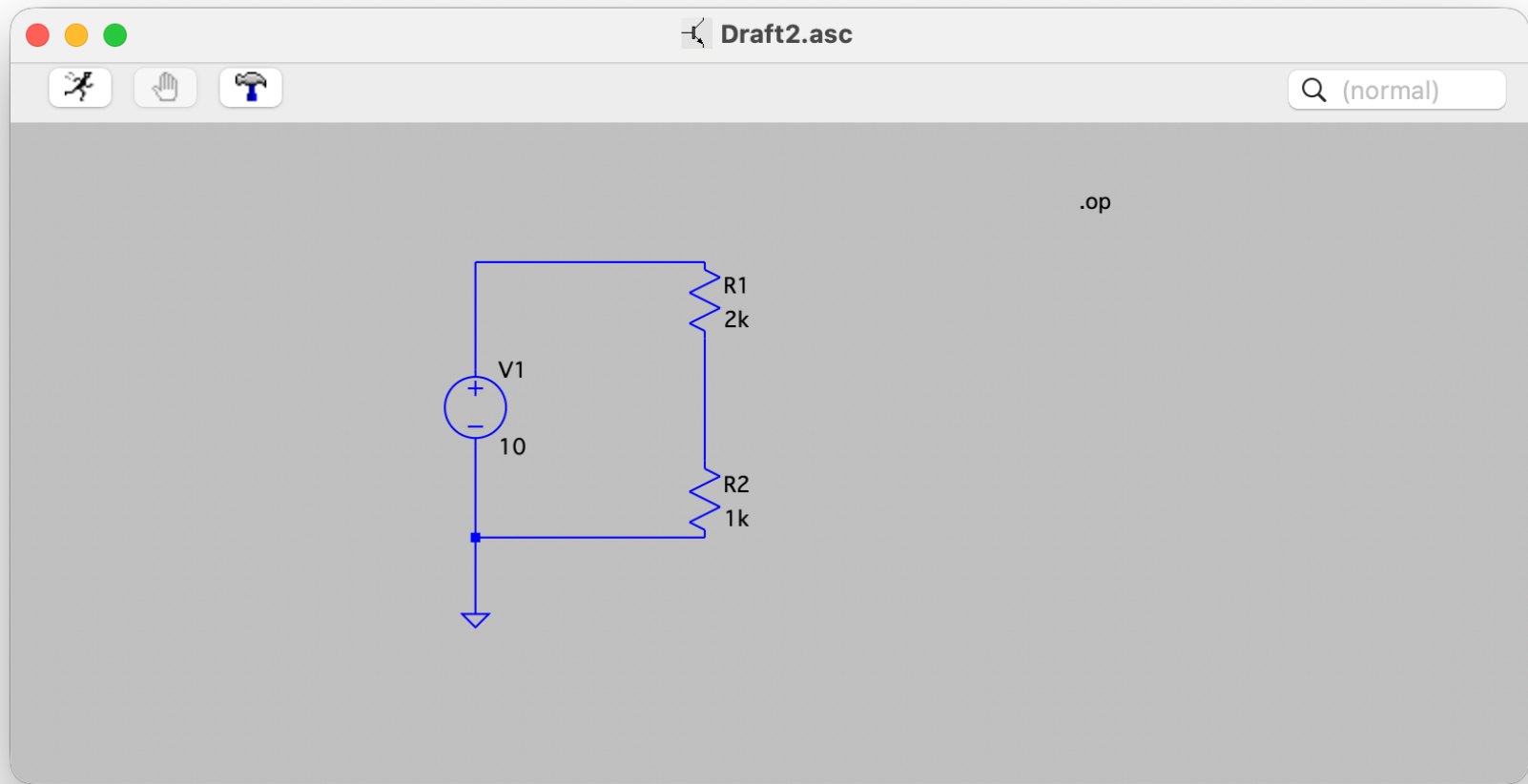
2.3.3 For a $V_{in} = 10V$, what will V_{out} be? In LTSpice, simulate the output voltage.

$$V_{out} = T \cdot V_{in} = \frac{1}{3} \cdot 10V = 10/3V \approx 3.33V$$



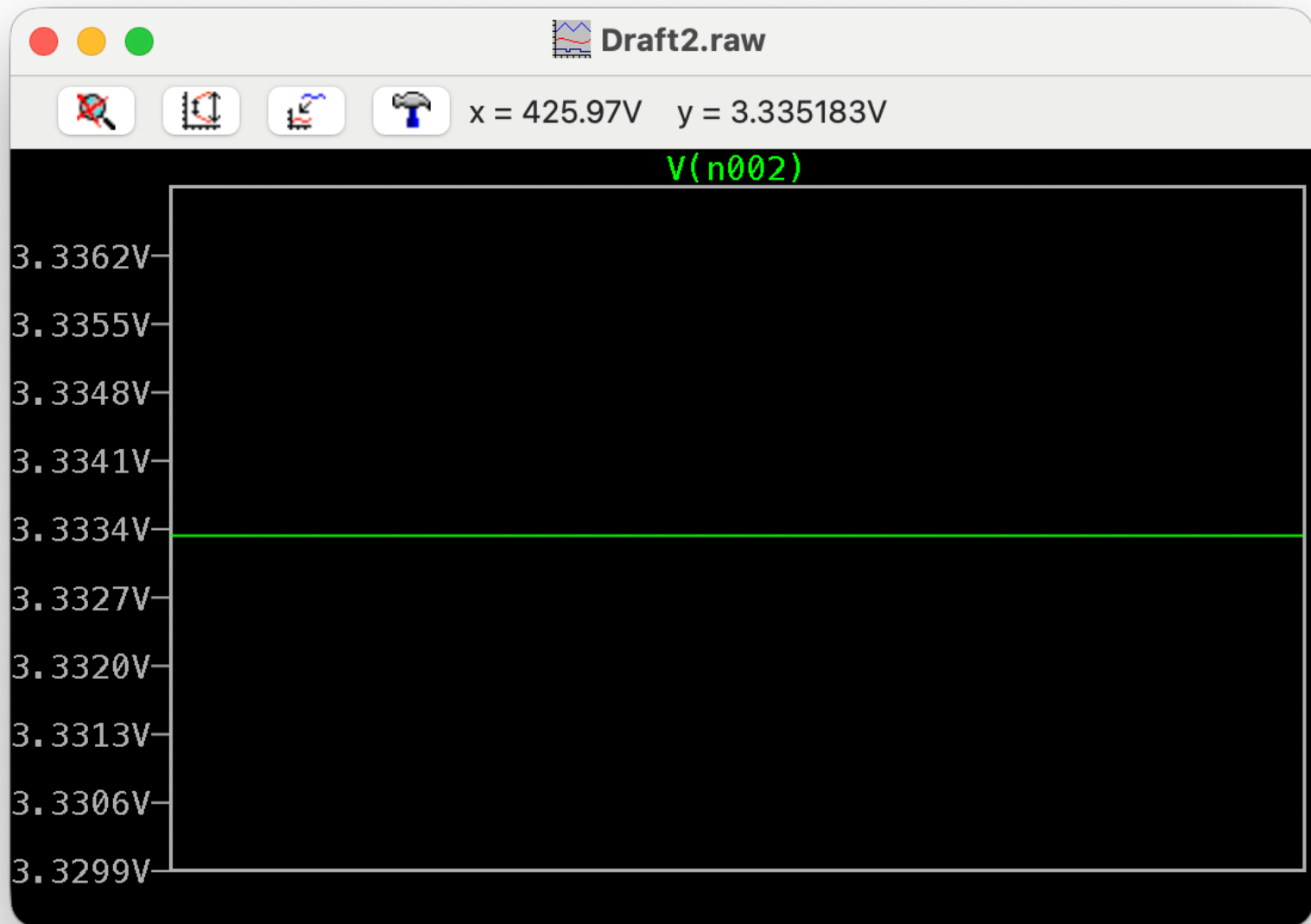

2.4 Input and Output Impedance

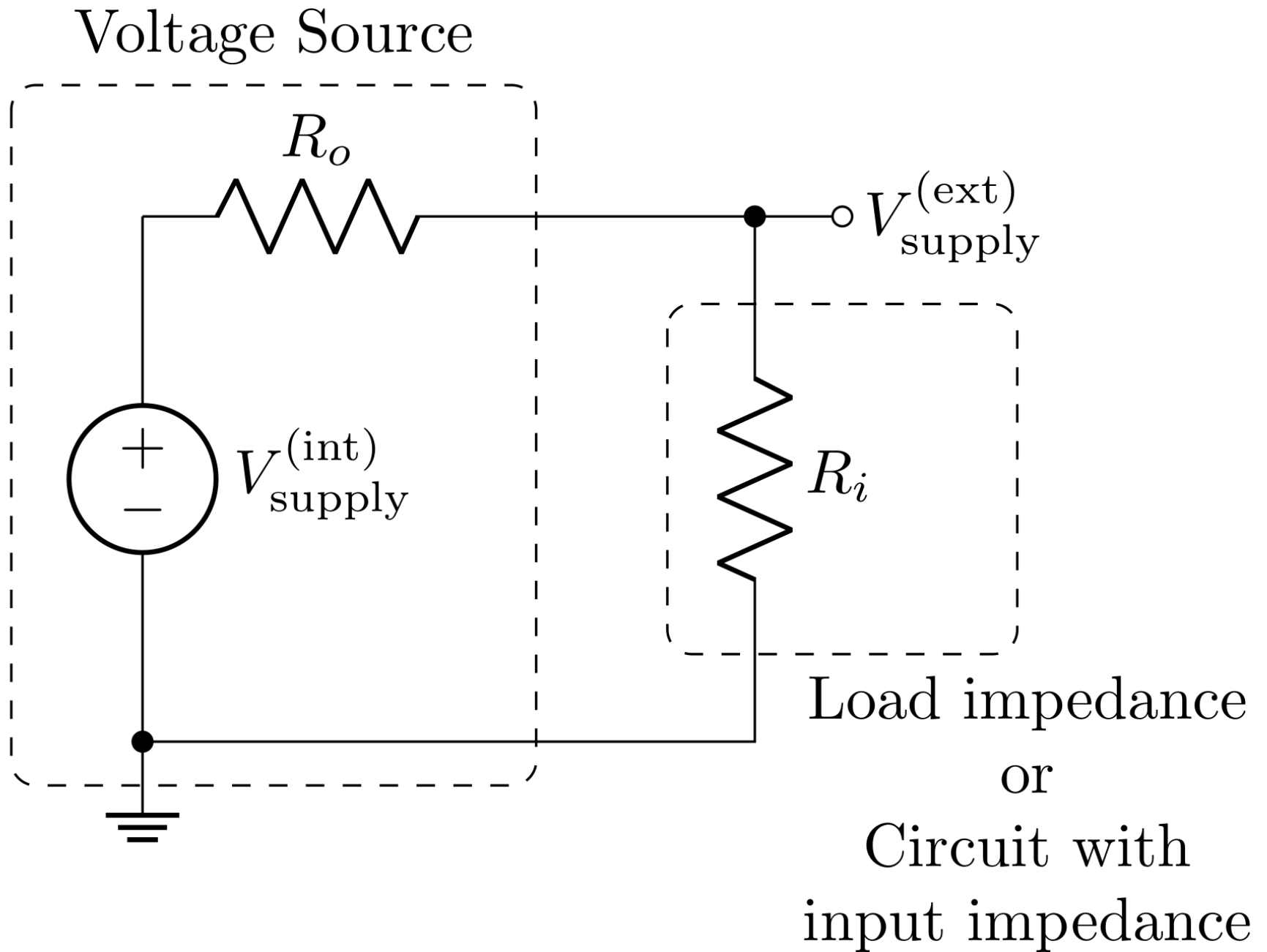

2.4.1 Confirm that the above transfer function from 2.3.1 is consistent with the transfer function $T = \frac{V_{\text{supply}}^{(\text{ext})}}{V_{\text{supply}}^{(\text{int})}} = \frac{R_i}{R_o + R_i}$

Treating the R_o and R_i resistors as being the voltage divider, we do indeed get $T = \frac{R_i}{R_o + R_i}$.

2.4.2 The power delivered is $P = I^2 R_i = IV_{supply}^{(ext)} = \frac{(V_{supply}^{(ext)})^2}{R_i}$. For a given R_o , find the R_i that maximizes the power delivered.

$$\begin{aligned}\frac{\partial P}{\partial R_i} &= \frac{\partial}{\partial R_i} (V_{supply}^{(ext)})^2 / R_i = \frac{\partial}{\partial R_i} (TV_{supply}^{(int)})^2 / R_i \\ &= \frac{\partial}{\partial R_i} \frac{\left(\frac{R_i}{R_o + R_i} V_{supply}^{(int)} \right)^2}{R_i} = - \frac{(R_i - R_o)(V_{supply}^{(int)})^2}{(R_i + R_o)^3} = 0 \\ &\implies R_o = R_i\end{aligned}$$


2.4.4 Plot P vs R_i from $R_i = 0\Omega$ to $R_i = 100\Omega$ using $V_{supply}^{(int)} = 1V$ with the following values of R_o on the same plot

- $R_o = 10\Omega$
- $R_o = 25\Omega$
- $R_o = 50\Omega$

```
In [40]: def power(r_o, r_i, v):
    r_i = np.asarray(r_i)
    return np.where(r_i == 0, 0.0, v**2 * r_i / (r_o + r_i)**2)


volt = 1
Ri = np.linspace(0, 100, 1000) # input impedance
output_impedances = (10, 25, 50)


fig, ax = plt.subplots(1, 1, figsize=(4, 3))
for Ro in output_impedances:
    ax.plot(Ri, power(Ro, Ri, volt), label=f'{Ro}  $\Omega$ ')
ax.set_xlabel('Input Impedance ( $\Omega$ )')
ax.set_ylabel('Power (W)')
ax.set_title('Power delivered from non-ideal voltage source')
ax.set_xticks(np.arange(0, 101, 10))
ax.set_xticks(np.arange(0, 101, 2), minor=True)
ax.set_xlim(0, 100)
ax.set_ylim(0, .026)
ax.minorticks_on()
ax.tick_params(axis='both', which='both', direction='in', top=True, right=True)
ax.legend(title="Output Impedance")
ax.grid(linestyle="dotted")
fig.tight_layout()
plt.show()
#fig.savefig('impedance_matching_plot.png', dpi=600, bbox_inches='tight')
```

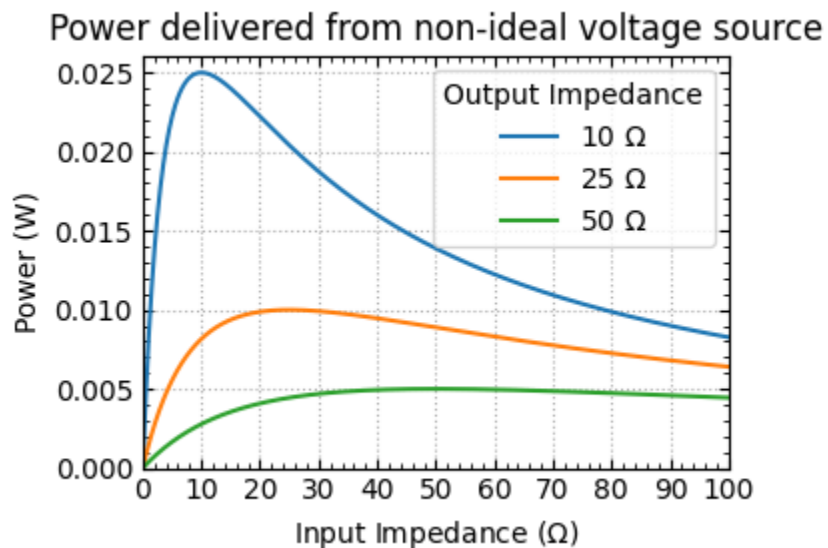

2.5 Voltage Divider with Non-ideal Power Supply

Real Power Supply

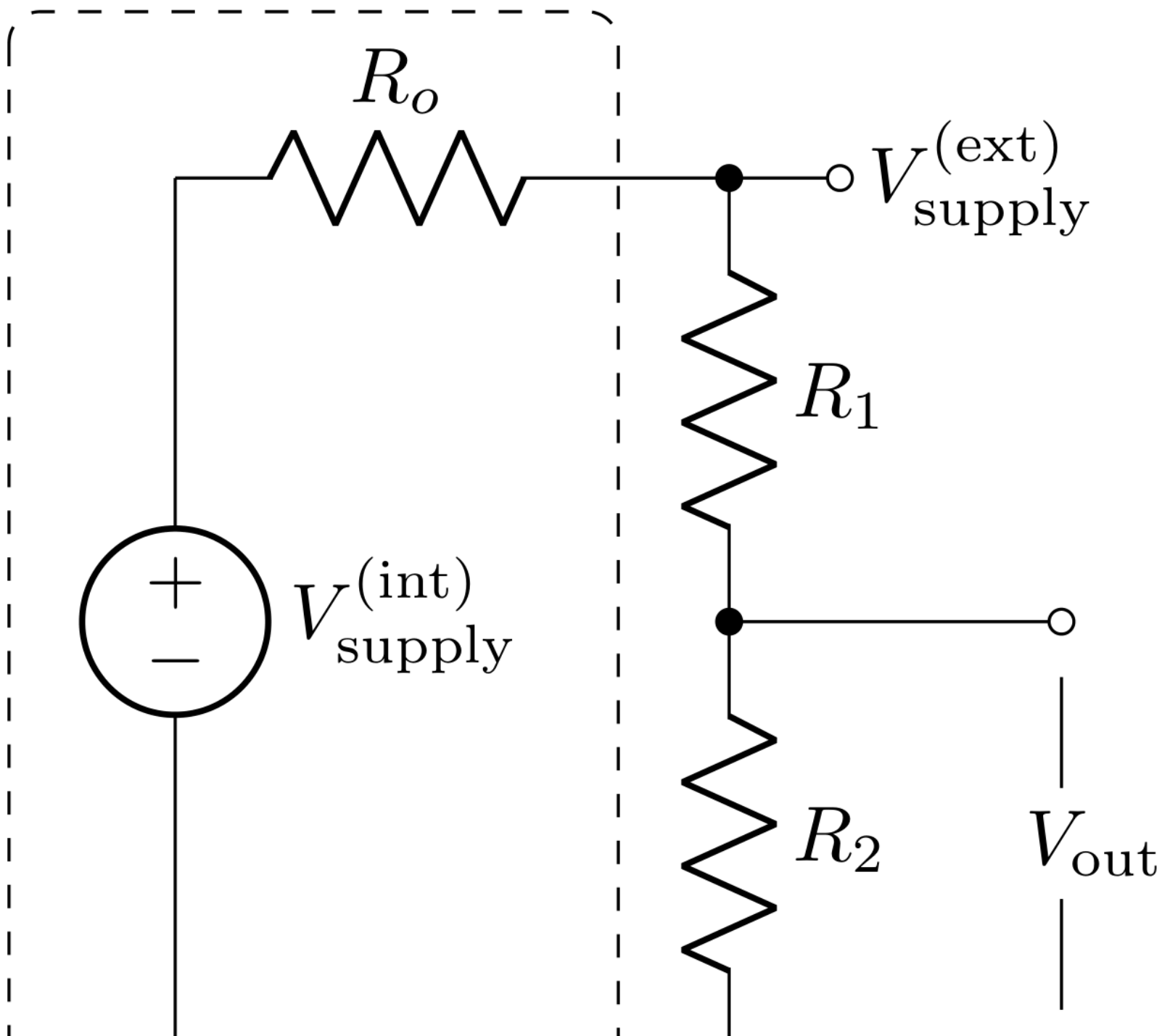

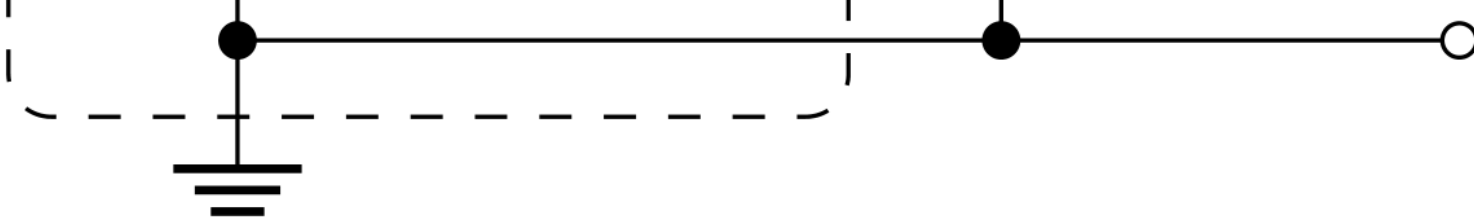

2.5.1 What is the input impedance of the voltage divider circuit?

This is just $R_1 + R_2$

2.5.2 The V_{in} of the voltage divider will be the $V_{supply}^{(ext)}$ from the power supply. Express V_{in} as a function of $V_{supply}^{(int)}$ and the resistor values.

$$V_{in} = V_{supply}^{(int)} \frac{R_1 + R_2}{R_o + R_1 + R_2}$$

2.5.3 Using the voltage divider, express V_{out} of the circuit with respect to $V_{supply}^{(int)}$ and the resistor value. Write a python function that computes the output voltage of a voltage divider with a non-ideal voltage supply.

$$V_{out} = V_{supply}^{(int)} \frac{R_2}{R_o + R_1 + R_2}$$

```
In [41]: def nonideal_voltage_divider_vout(V_int: float, R_o: float, R1: float, R2: float) -> float:
        """
        Compute V_out for a voltage divider fed by a non-ideal supply.
        V_out = V_int * R2 / (R_o + R1 + R2)

        Args:
            V_int: internal supply voltage (V_supp^{(int)})
            R_o: source output impedance
            R1: top resistor of divider
            R2: bottom resistor of divider


        Returns:
            V_out (float or numpy array)
        """
        denom = R_o + R1 + R2
        try:
            return V_int * R2 / denom
        except ZeroDivisionError:
            return 0.0
```


2.5.4 For an ideal voltage divider ($R_o = 0\Omega$) having $R_1 = 100\Omega$ and $R_2 = 50\Omega$ or $R_1 = 2k\Omega$ and $R_2 = 1k\Omega$ or $R_1 = 200k\Omega$ and

$R_2 = 100k\Omega$ will have the same transfer function. Predict V_{out} when the ideal voltage source is set to $10V$. Build these circuits in LTSpice.

$$V_{out} = 10V \cdot \frac{R_2}{R_1 + R_2}$$

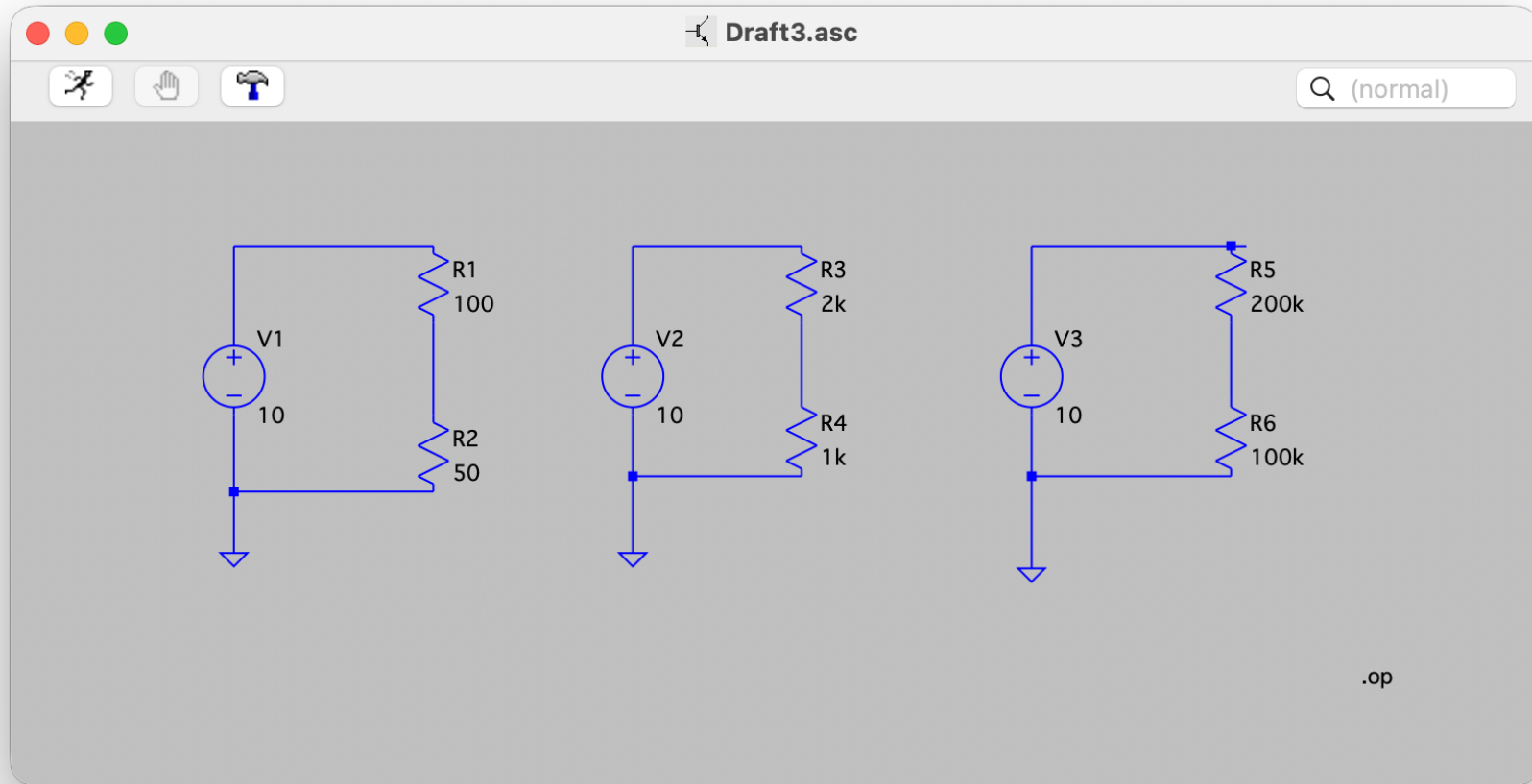- $R_1 = 100\Omega$ and $R_2 = 50\Omega$ $V_{out} = 10V \cdot \frac{50\Omega}{150\Omega} \approx 3.33V$
- $R_1 = 2k\Omega$ and $R_2 = 1k\Omega$ $V_{out} = 10V \cdot \frac{1k\Omega}{3k\Omega} = 3.33V$
- $R_1 = 200k\Omega$ and $R_2 = 100k\Omega$ $V_{out} = 10V \cdot \frac{100k\Omega}{300k\Omega} = 3.33V$



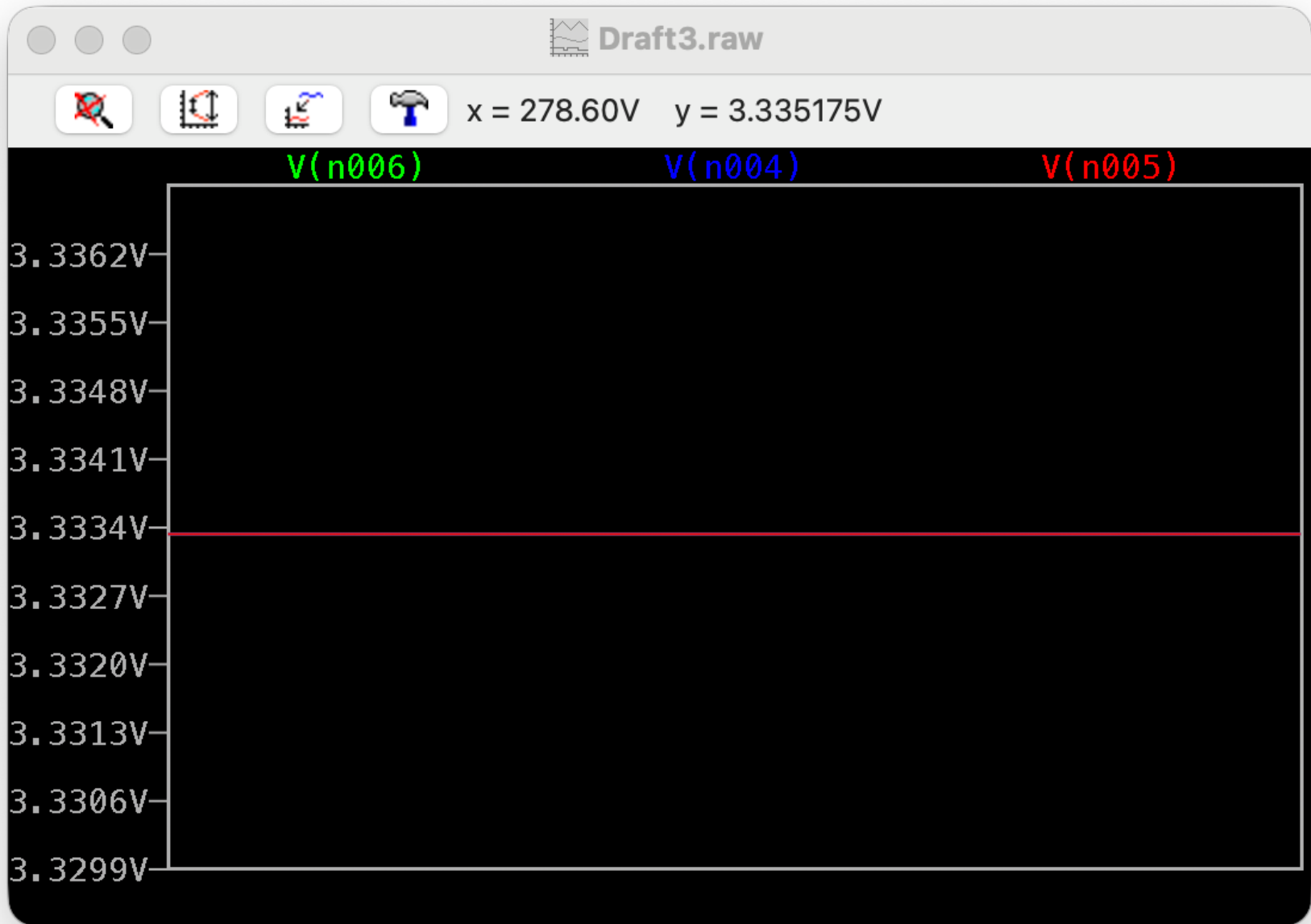


All the values match exactly.

2.5.5 What is V_{out} for each 2.5.4, but with an output impedance of $R_o = 50\Omega$?

- $R_1 = 100\Omega$ and $R_2 = 50\Omega$ $V_{out} = 10V \cdot \frac{50\Omega}{200\Omega} \approx 2.5V$


- $R_1 = 2k\Omega$ and $R_2 = 1k\Omega$ $V_{out} = 10V \cdot \frac{1k\Omega}{3050\Omega} = 3.27V$
- $R_1 = 200k\Omega$ and $R_2 = 100k\Omega$ $V_{out} = 10V \cdot \frac{100k\Omega}{300,050\Omega} = 3.33V$

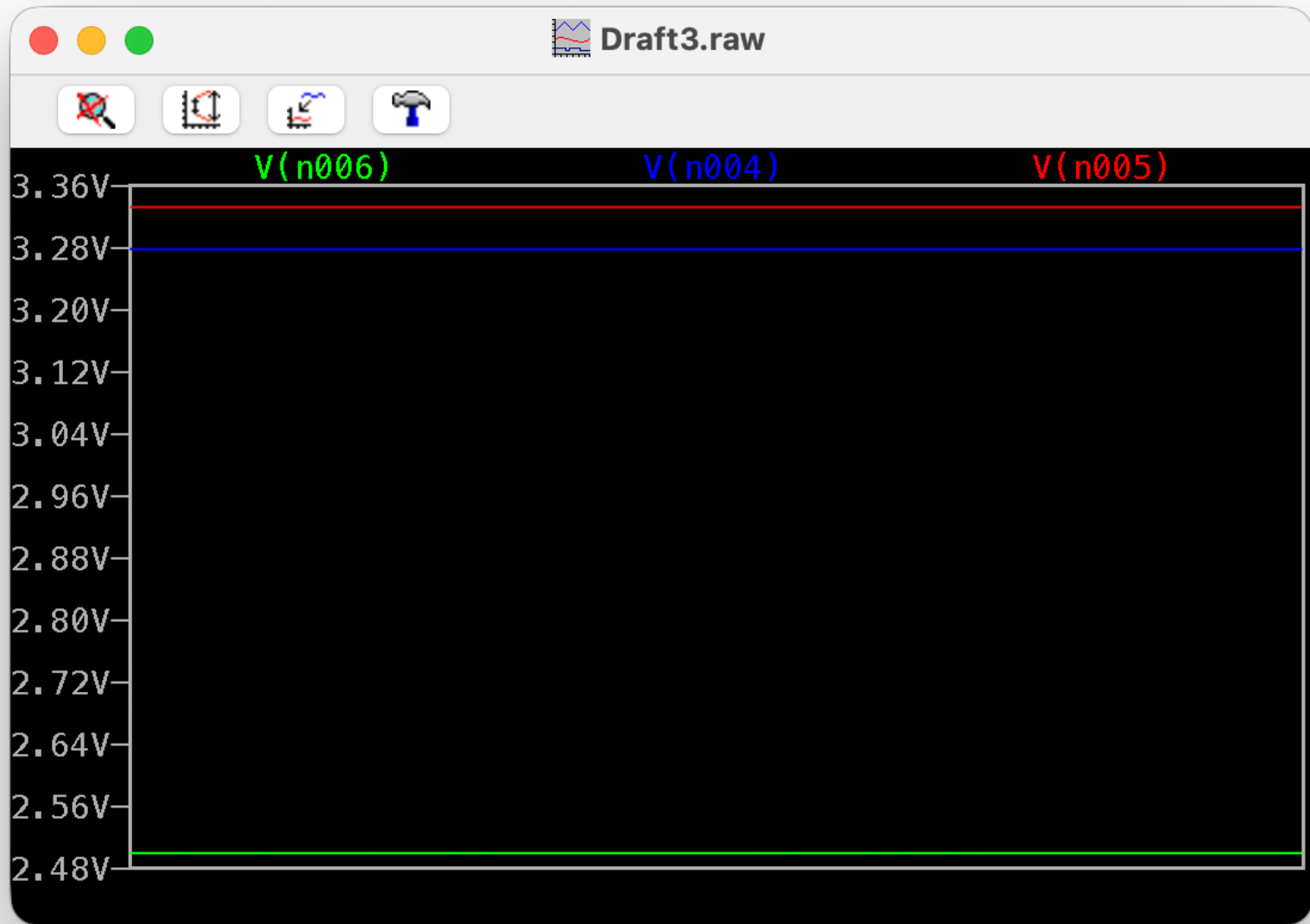Circuit is the same with 50Ω impedance on the voltage source. Simulated values match calculation exactly.



- Compare the output voltage of the voltage divider with an ideal voltage source vs a non-ideal voltage source.
 - When the voltage source is ideal, it provides a much more stable voltage than if it is non-ideal. Non-ideal voltage sources mess with the voltage of the output circuit and must be accounted for if you need an accurate measurement.
- How does the input impedance of the voltage divider ($R_1 + R_2$) impact the non-ideal circuit compared to the ideal circuit?
 - If the input impedance is much much larger than the resistance of the voltage source, you get behavior that approximates an ideal voltage source. However, when the input impedance near or on the same order of magnitude, the behavior becomes much less stable.
- What condition should be met such that both the ideal and non-ideal voltage source models sufficiently agree?
 - In order to keep the ideal and non-ideal models in sufficient agreement, we require $R_o \ll (R_1 + R_2)$.

Impacts of Parallel Impedances

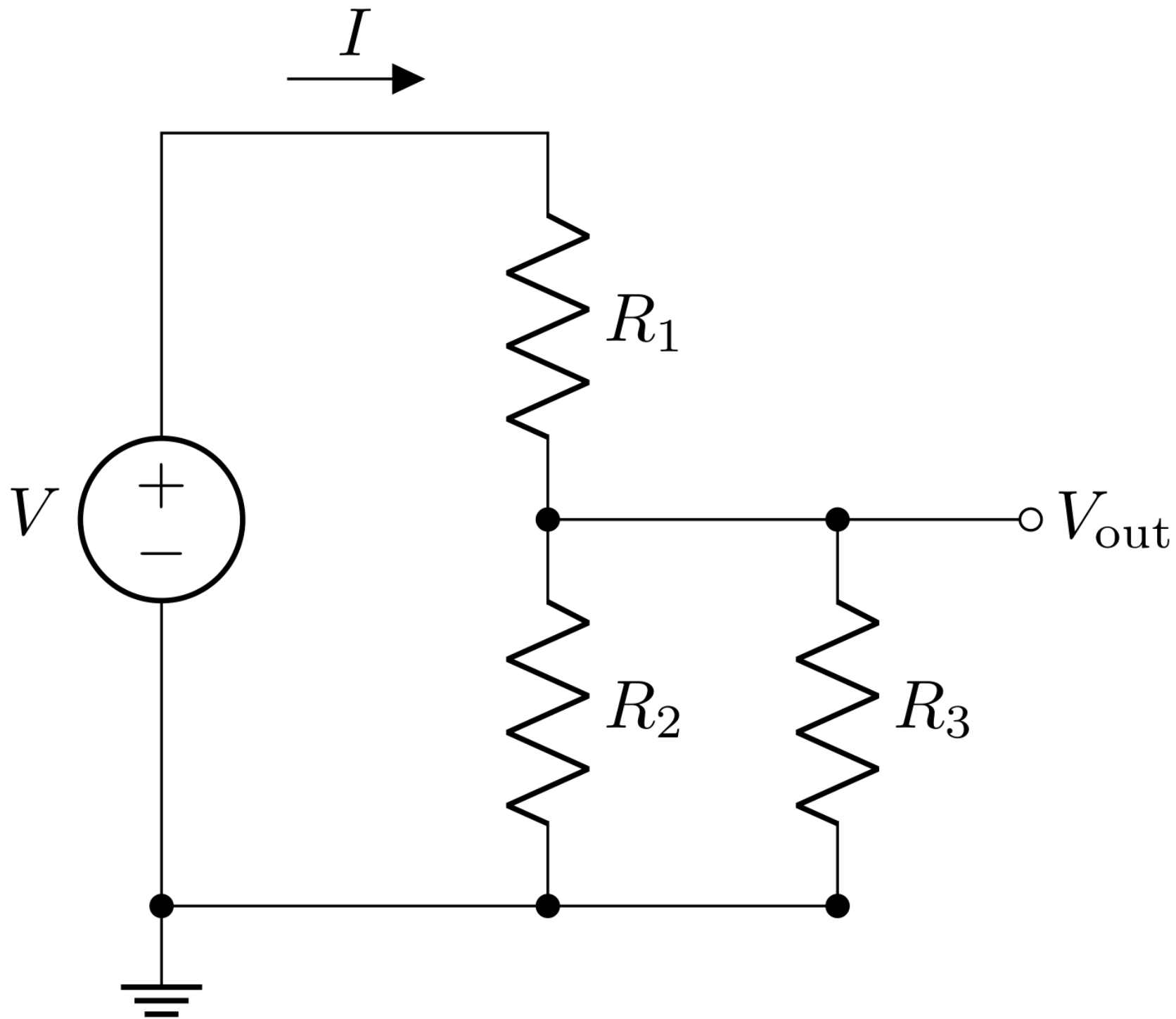

2.6.1 Rearrange $T = \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$ for R_3 .

$$TR_1 R_2 + TR_1 R_3 + TR_2 R_3 = R_2 R_3$$

$$TR_1 R_2 = (R_2 - TR_1 - TR_2) R_3$$


$$R_3 = \frac{TR_1 R_2}{R_2 - TR_1 - TR_2}$$

$$R_3 = \frac{TR_1 R_2}{R_2 - T(R_1 + R_2)}$$

```
In [42]: def R_3(V_in, V_out, R_1, R_2):
        """
        Compute the required load resistance R_3 to achieve a desired V_out
        from a voltage divider with input voltage V_in and resistors R_1 and R_2.

        Args:
            V_in: input voltage
            V_out: desired output voltage
            R_1: top resistor of divider
            R_2: bottom resistor of divider
        Returns:
            R_3 = TR_1R_2 / (R_2 - T(R_1 - R_2)) where T = V_out / V_in
        """
        T = V_out / V_in
        numerator = T * R_1 * R_2
        denominator = R_2 - T * (R_1 - R_2)
        try:
            return numerator / denominator
        except ZeroDivisionError:
            return np.inf
```

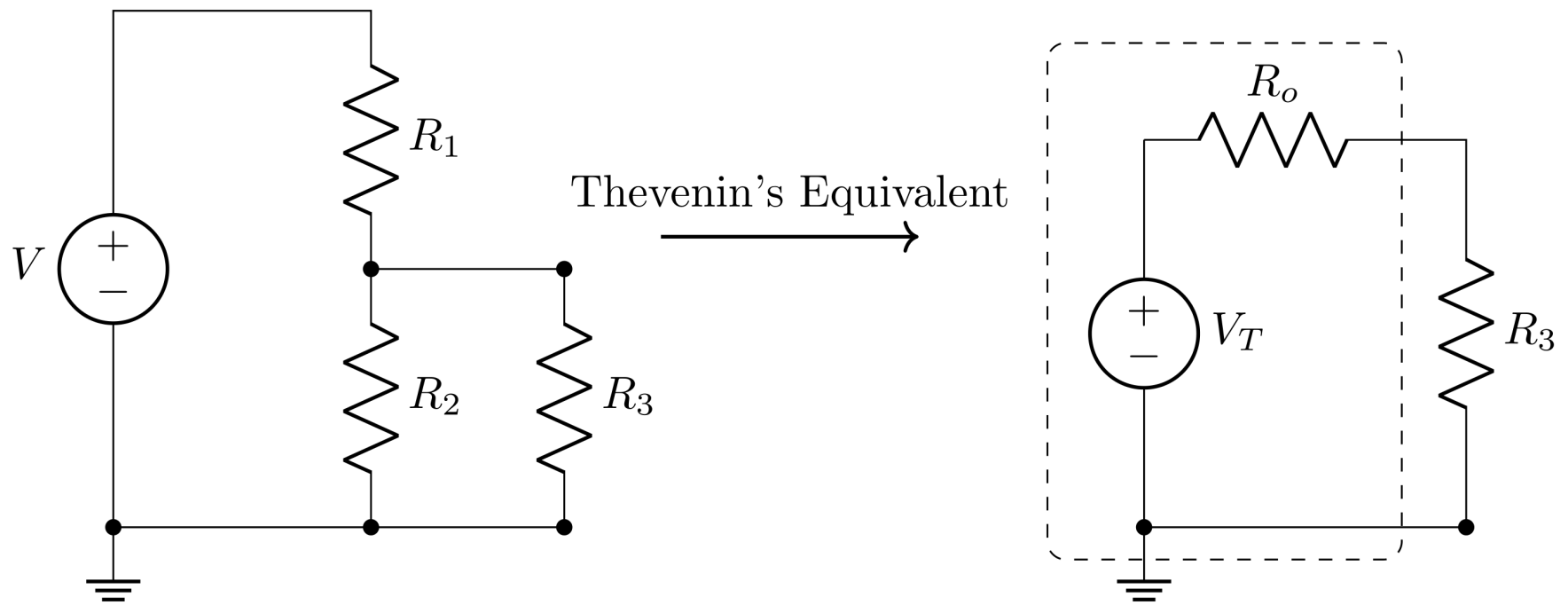2.7 Thevenin's Theorem and the Voltage Divider



$$V_T = V_{in} \frac{R_2}{R_1 + R_2}$$

$$R_o = \frac{R_1 R_2}{R_1 + R_2}$$

2.7.1 Use the result of 2.6.1 to show that the voltage across R_3 is the same as the voltage predicted by the Thevenin equivalent circuit.

We have $V_{R_3} = V_T \cdot \frac{R_3}{R_o + R_3}$, so plugging in the definitions above, and 2.6.1

$$V_{R_3} = \left(V_{in} \frac{R_2}{R_1 + R_2} \right)^2 \cdot \frac{R_3}{\frac{R_1 R_2}{R_1 + R_2} + R_3}$$

then multiply both top and bottom by $R_1 + R_2$

$$V_{R_3} = V_{in} \cdot \frac{R_2 R_3}{R_1 R_2 + R_3 (R_1 + R_2)}.$$

Now the transmission coefficient for this problem is $T = \frac{V_{R_3}}{V_{in}}$, so from above

$$T = \frac{R_2 R_3}{R_1 R_2 + R_3(R_1 + R_2)}$$

which, after some algebra, gives

$$R_2 R_3 = T R_1 R_2 + T R_3(R_1 + R_2)$$

$$R_2 R_3 - T R_3(R_1 + R_2) = T R_1 R_2$$

$$R_3(R_2 - T(R_1 + R_2)) = T R_1 R_2$$

$$R_3 = \frac{T R_1 R_2}{R_2 - T(R_1 + R_2)}$$

which is exactly what was computed above.